

EC102 - UNIT 2 NOTES

Combinational Logic Circuits

College Student Study Portal - Comprehensive Lecture & Revision Notes

Key Topics Covered in this Unit:

Half adder, Full adder, Parallel adder, Subtractors, Encoders, Priority encoders, Multiplexers (MUX) & Demultiplexers.

Summary & Key Concepts:

1. Theoretical Foundations & Fundamental Definitions
2. Step-by-Step Analytical Solutions and Problem Sets
3. Formula Sheet & Fast Revision Guide for Midterm and Semester Exams
4. Previous University Exam Questions with Model Answers

Generated for Student Hub Portal | Keep learning and excel in your exams!